

GATE -BM 16

EE23BTECH11057 - Shakunaveti Sai Sri Ram Varun

Question: For the circuit given below, choose the angular frequency ω_0 at which voltage across capacitor has maximum amplitude?

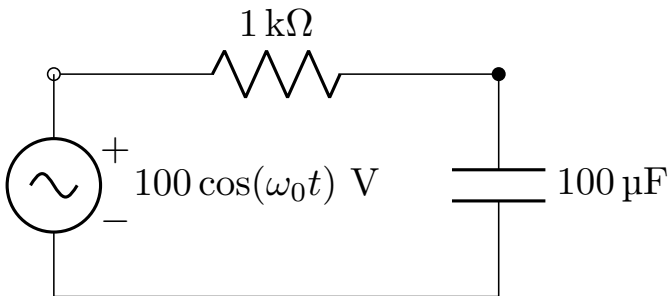


Fig. 1. circuit

- (A) 1000
- (B) 100
- (C) 1
- (D) 0

(GATE BM 2023)