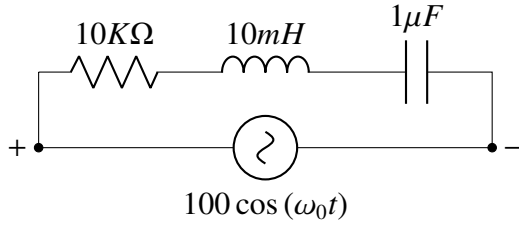


# GATE-2023 BM Q-42

EE23BTECH11207 -KAILASH.C\*

In the circuit shown below, it is observed that the amplitude of voltage across the resistor is the same as the amplitude of the source voltage. What is the angular frequency  $\omega_0$  (in rad/s)?




- (A)  $10^4$   
 (B)  $10^3$   
 (C)  $10^3\pi$   
 (D)  $10^4\pi$

**Solution:**

Symbols	Parameters	Value
R	Resistance	$10K\Omega$
L	Inductance	$10mH$
C	Capacitance	$1\mu F$
$\omega_0$	Angular Frequency	
$V_s$	Source Voltage	

TABLE 0  
PARAMETER TABLE

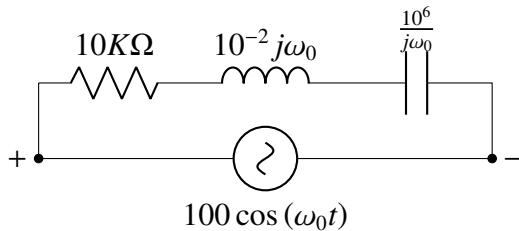

We have:

$$V_R = V_s \quad (1)$$

Using KVL:

$$V_s = V_R + V_C + V_L \quad (2)$$

By using (1) in (2):

$$V_C = -V_L \quad (3)$$

$$X_C = -X_L \quad (4)$$

$$\frac{1}{j\omega_0 C} = -j\omega_0 L \quad (5)$$

$$\frac{1}{LC} = -j^2 \omega_0^2 \quad (6)$$

$$\omega_0^2 = \frac{1}{LC} \quad (7)$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad (8)$$

$$= \frac{1}{\sqrt{10^{-2} \times 10^{-6}}} \quad (9)$$

$$= \frac{1}{10^{-4}} \quad (10)$$

$$= 10^4 \text{ rad/s} \quad (11)$$

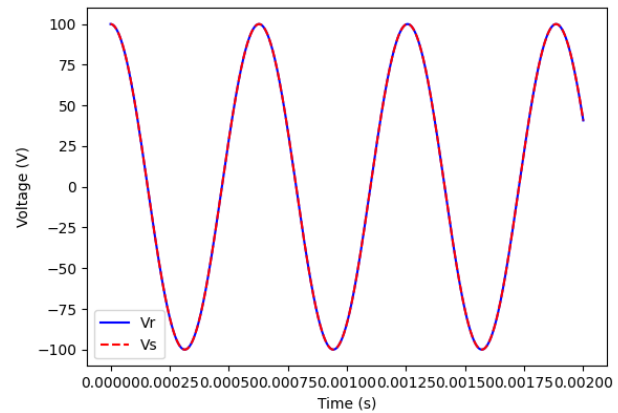


Fig. 0. Voltage across Resistor and Source voltage